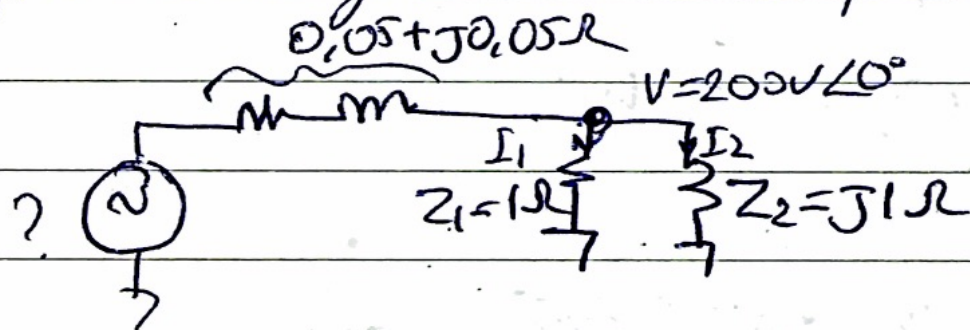


# Exercises

## AC Systems

Two loads  $Z_1 = 1 \Omega$  (purely resistive) and  $Z_2 = j1 \Omega$  purely inductive are connected across a source through a transmission line with an impedance of  $Z_{line} = 0.05 + j0.05 \Omega$ .  
If the voltage of the loads is  $200V_{rms}$ , find the voltage, current and complex power of the source.



$$\vec{I}_1 = 200A \angle 0^\circ \quad \vec{I}_2 = 200A \angle -90^\circ \quad \vec{I}_1 + \vec{I}_2 = 200\sqrt{2} \angle -45^\circ$$

$$\text{or } Z_1 // Z_2 = 1 // j1 = 0.5 + j0.5 \Rightarrow \vec{I}_L = \frac{200}{0.5 + j0.5} = 200\sqrt{2} \angle -45^\circ$$

$$\frac{j1}{(1+j)(1-j)} = \frac{j+1}{2} \Rightarrow \underline{\underline{200 - j200A}}$$

Real power is only consumed by resistive elements  $\Rightarrow P_{Z1} = \frac{V^2}{R} = \frac{200^2}{1} = \underline{\underline{40kW}}$

Reactive power is "exchanged" by inductive elements  $Q_{Z1} = \frac{V^2}{X_L} = 40kVAR$

formal way

$$S_L = V_L \cdot \vec{I}_L^* = 200(200 + j200) = \underbrace{40kW}_{\text{consumed by } Z_1} + j \underbrace{40kVAR}_{\text{exchanged by } Z_2}$$

Source voltage:

$$V_s = \vec{V}_L + Z_{line} \cdot \vec{I}_L$$

$$= 200 \angle 0^\circ + \underbrace{(0.05 + j0.05)}_{\sqrt{2} \cdot 0.05 \angle 45^\circ} \cdot 200 \sqrt{2} \angle -45^\circ$$

$$= 200 + 20 = \underline{\underline{220V}}$$

$$\rightarrow 200 + (0.05 + j0.05) \cdot \cancel{200 \sqrt{2}} \cdot (200 - 200j)$$

$$200 + 10 - 10j + 10j + 10$$

$$= \underline{\underline{220V}}$$

$$S_{source} = V_s \vec{I}_s^* = 220 \times 200 \sqrt{2} \angle 45^\circ$$

$$= \underline{\underline{44kW + j44kVAR}}$$

$\left. \begin{array}{l} +4kW \\ +4kVAR \end{array} \right\}$  for the transmission line.